

(PClk). The R4650 does not generate any output clock. The MasterClock should be used as the system control logic clock. The R4650 guarantees that the interface signals with the external system logic will be sampled using the rising edge of MasterClock. Figure 2 illustrates the internal clock tree of the R4650.

An advantage of the R4650 is that the MasterClock frequency may be kept small. Similarly, the absence of output clocks from the R4650 reduces the power consumption of the device. This architecture allows several systems to synchronize using a single input clock at any frequency without being locked by the clocks provided by the CPU. This is particularly advantageous for backplane applications where the input clock is provided from the backplane to several plugged-in cards.

GENERATING R4600-COMPATIBLE CLOCKS

Systems using the R4650 can reuse the logic and ASICs already developed to work with the R4600. This mechanism requires the generation of MasterOut, SyncOut, RClock and TClock, or alternatively, a subset of these according to the system requirements. The functionality of the different clocks is explained more in detail in the *"IDT79R4600 Hardware User's Manual"*.

The clock distribution tree has to be implemented at the input of the R4650. The R4600 clock generation is illustrated in Figure 3. In this case, a buffer is used to delay the input clock to the R4650. The output of the buffer is equivalent to TClock, MasterOut and SyncOut. The input of the buffer is equivalent to RClock. For a tight delay between RClock and TClock, it is better to use a buffer that has a very narrow window for the min and the max input to output delays. An example of such a clock buffer is the Motorola MC10H645 buffer, which guarantees a single nanosec difference between the min and the max delays.

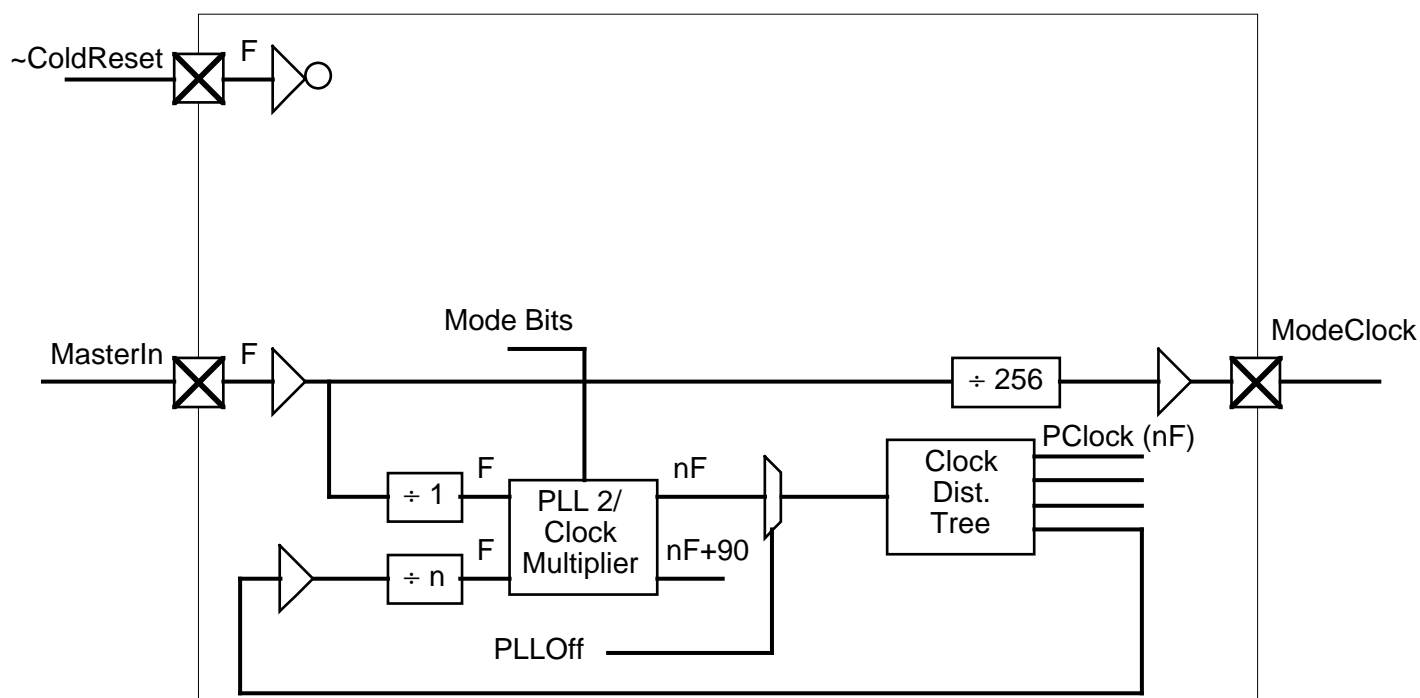


Figure 2. R4650 Clock Distribution Tree and PLL

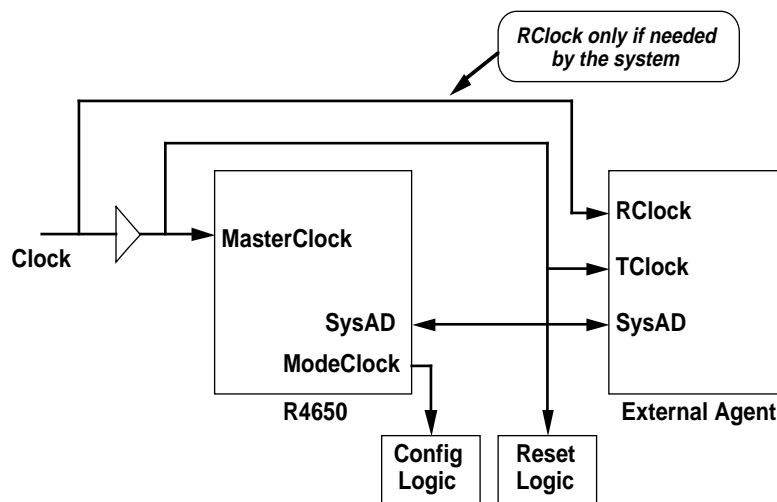


Figure 3. Generating R4600-Compatible Clocks

It is also important to note that in systems using only the R4650, the SyncOut to SyncIn path is irrelevant, since neither the R4650 nor the system logic use these clocks. The MasterOut could be relevant, depending on the system architecture.

DESIGNING A SYSTEM THAT SUPPORTS BOTH CPUs

It is possible to design a single system to support either the R4600 or the R4650 on a single PCB board. The same design allows using the R4600 for high performance applications, while using the R4650 to serve the medium performance segment of the market. This approach preserves the investment in the ASIC development, the system logic, the system

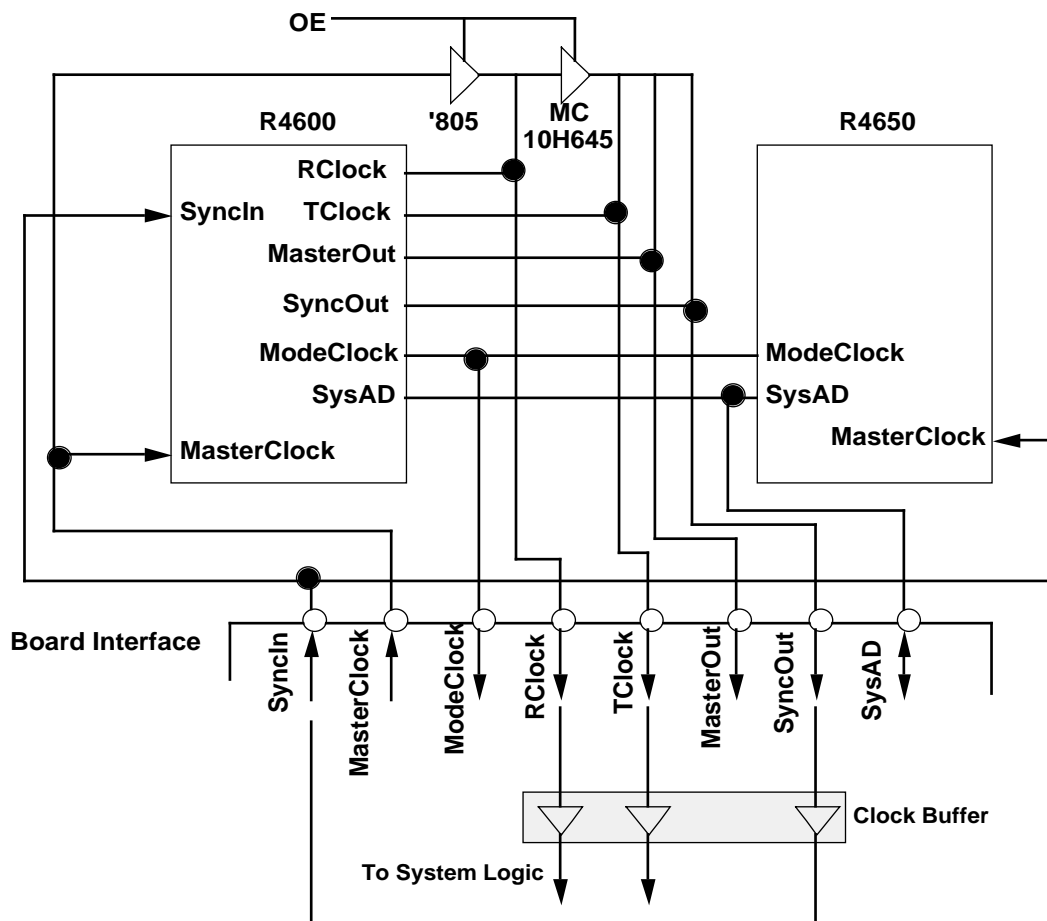


Figure 4. Single System With R4600 and R4650

software and so on. Figure 4 illustrates the block diagram for a system that can support both CPUs on the single PCB.

In this implementation, the clock from the external oscillator, MasterClock, is fed as the input clock to the R4600. It is also fed to the clock distribution circuitry that generates RClock, TClock, MasterOut and SyncOut to be used when the R4650 is used. It is important to note that only one CPU should be plugged-in at any onetime. The clock distribution circuitry is tri-statable when the R4600 is used, since it produces these clocks.

The SyncOut clock is routed on the PCB and returned as SyncIn. The SyncIn clock is fed to the R4600 to align the internal clocks used to sample the system interface, with the RClock and TClock seen by the system logic. In the case of the R4650 the SyncIn clock is used as the input MasterClock to the CPU. This ensures that the input clock to the R4650 is aligned to the system clocks (RClock and TClock) that are generated by the clock distribution circuitry.

THE 79S461

The 79S461 is a small module that supports both the R4600 and the R4650 on a single PCB. It plugs into the PGA socket of the R4600 on any design. It allows the system designer to evaluate the performance of either CPU in the system without modifications to the existing design. Figure 5 illustrates the block diagram of the 79S461. In addition, the schematics of the S461 board are attached to the end of this App Note to provide a better understanding in converting from one clock architecture to the other.

CONCLUSION

It is relatively easy to adapt a design that is based on the R4600 to support the R4650 on a single PCB. This approach offers a great flexibility in selecting the appropriate CPU for the level of performance needed without redesigning the system. The same design allows using the R4600 for high performance applications, while using the R4650 to serve the medium performance segment of the market.


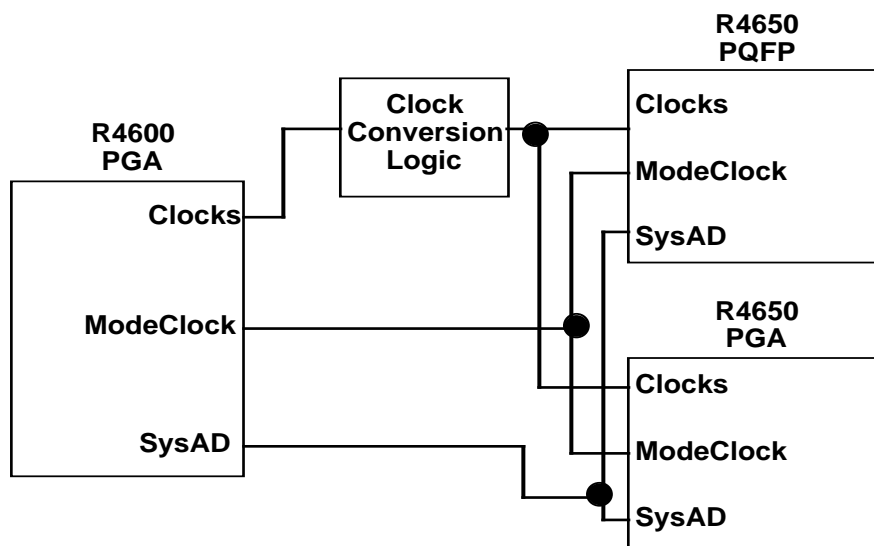


Figure 5. 79S461 Block Diagram

P3-MODULE PGA PLUG

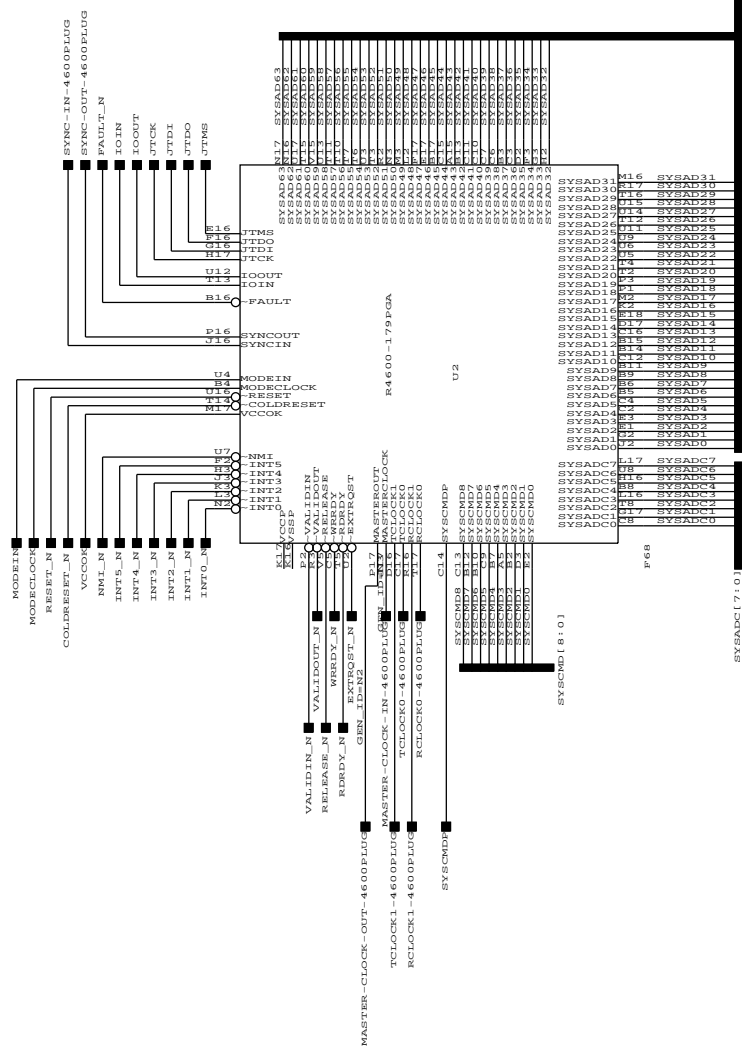


INTEGRATED DEVICE TECHNOLOGY, INC.


179 PGA R4600 PLUG

SIZE	DWG NO.	REV
CR	S461	1.0
DATE: 3-1-1995_10:57		SHEET 1 OF 4

P3-MODULE-PGA & PQFP-SOCKETS

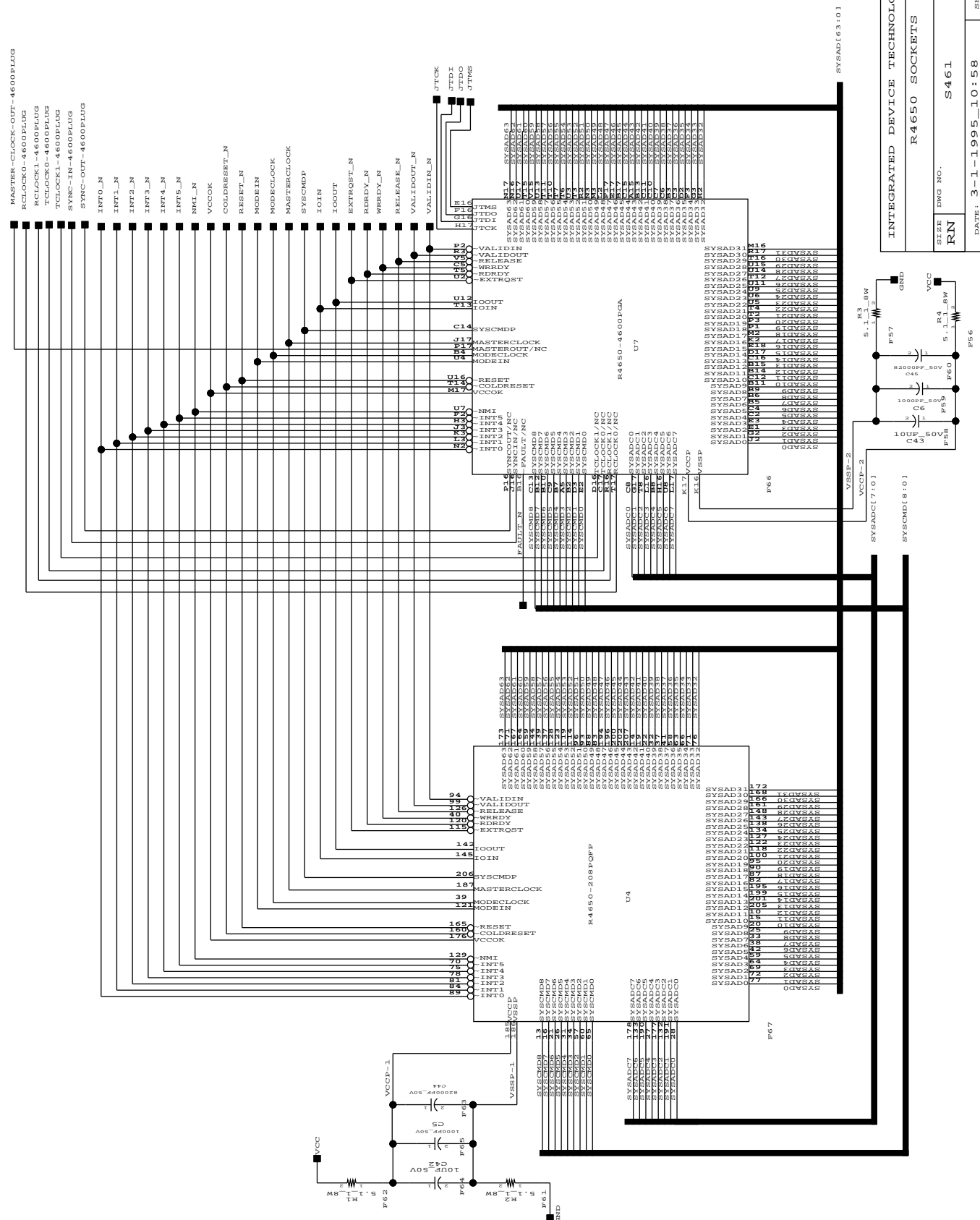

P3-MODULE-CLOCK-DISTRIBUTION & BUFFERING

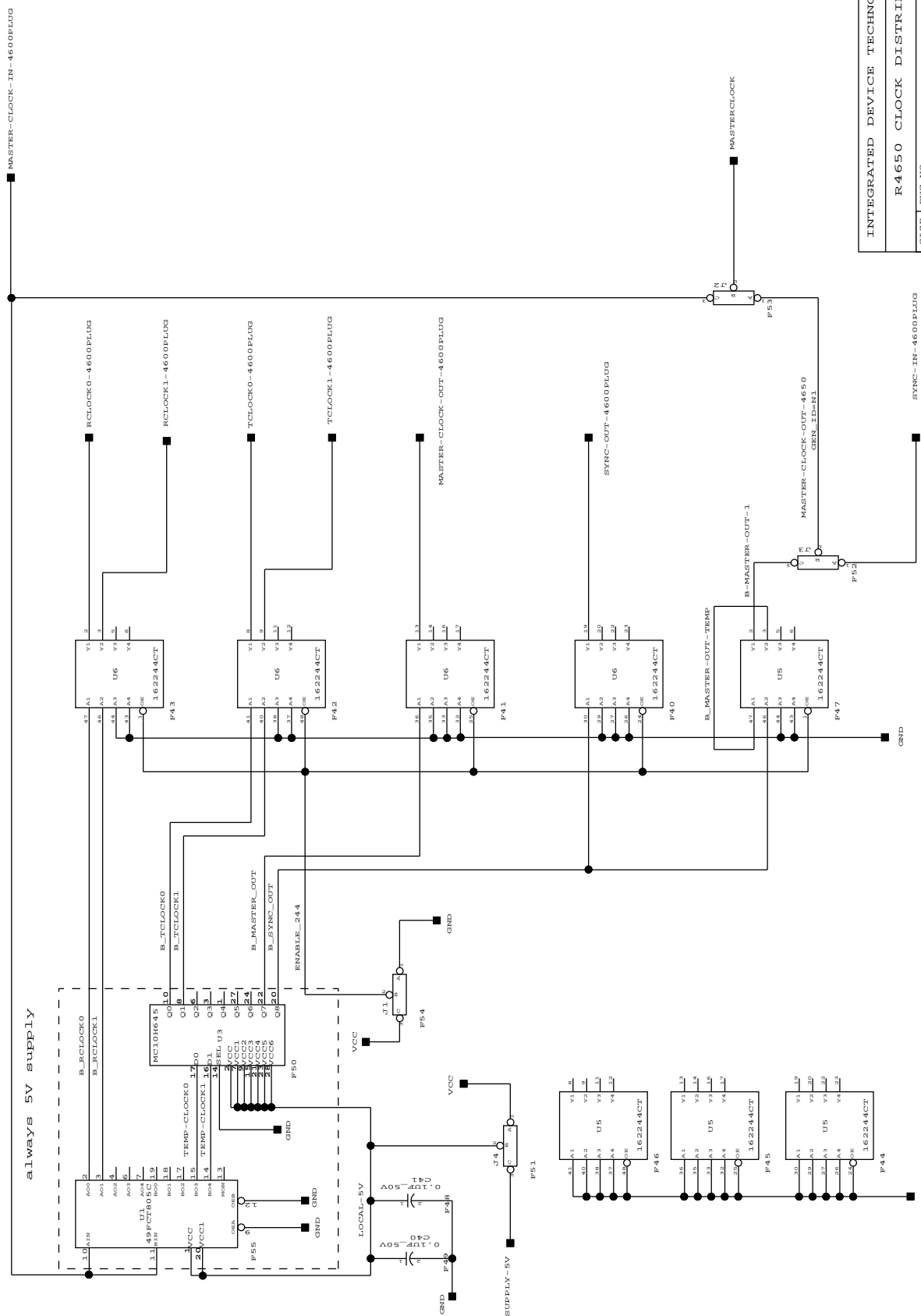


INTEGRATED DEVICE TECHNOLOGY, INC.


R4650 CLOCK DISTRIBUTION

SIZE	DWG NO.	REV
NRN	S461	1.0

DATE: 3-1-1995_10:59	SHEET 3 OF 4
----------------------	--------------

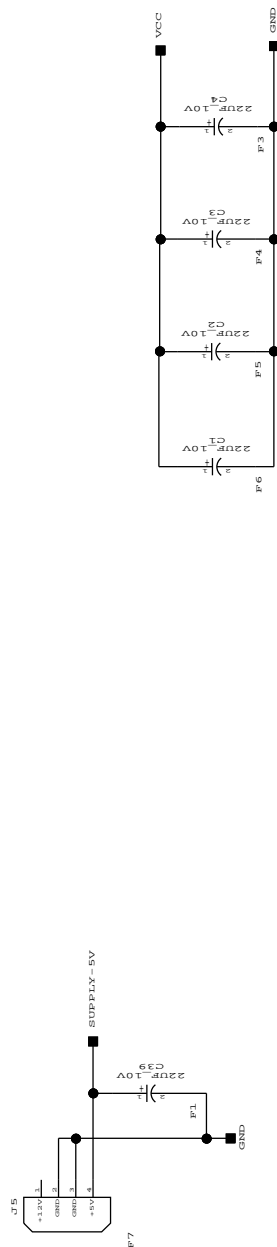

P3_MODULE CPU BYPASS CAPACITORS

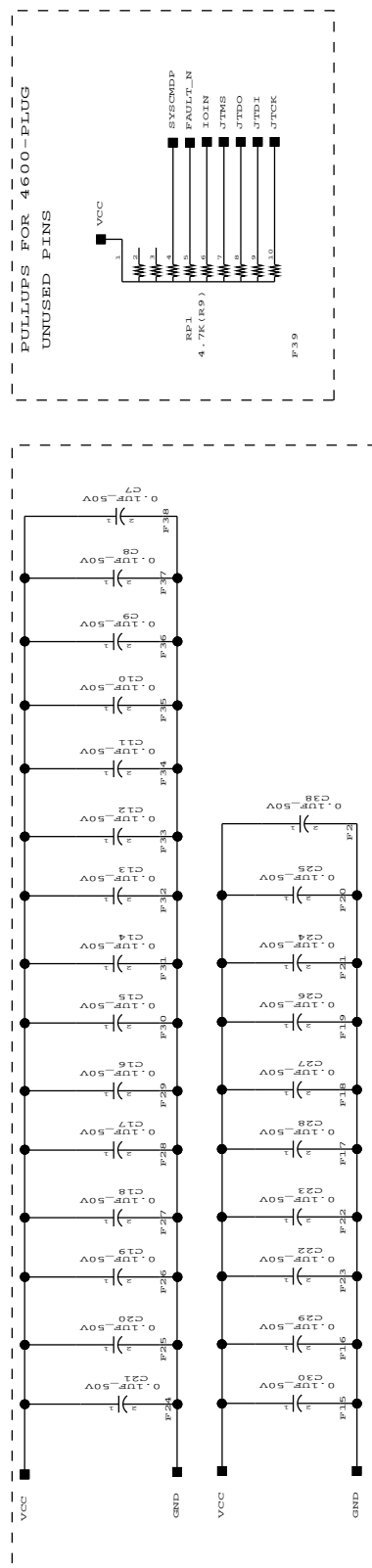

INTEGRATED DEVICE TECHNOLOGY, INC.

CAPACITORS

SIZE CR	DWG NO. S461	REV 1.0
DATE: 3-1-1995_10:42		SHEET 4 OF 4

IMPORTANT NOTICE AND DISCLAIMER

RENESAS ELECTRONICS CORPORATION AND ITS SUBSIDIARIES ("RENESAS") PROVIDES TECHNICAL SPECIFICATIONS AND RELIABILITY DATA (INCLUDING DATASHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS OR IMPLIED, INCLUDING, WITHOUT LIMITATION, ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for developers skilled in the art designing with Renesas products. You are solely responsible for (1) selecting the appropriate products for your application, (2) designing, validating, and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, or other requirements. These resources are subject to change without notice. Renesas grants you permission to use these resources only for development of an application that uses Renesas products. Other reproduction or use of these resources is strictly prohibited. No license is granted to any other Renesas intellectual property or to any third party intellectual property. Renesas disclaims responsibility for, and you will fully indemnify Renesas and its representatives against, any claims, damages, costs, losses, or liabilities arising out of your use of these resources. Renesas' products are provided only subject to Renesas' Terms and Conditions of Sale or other applicable terms agreed to in writing. No use of any Renesas resources expands or otherwise alters any applicable warranties or warranty disclaimers for these products.

(Disclaimer Rev.1.0 Mar 2020)

Corporate Headquarters

TOYOSU FORESIA, 3-2-24 Toyosu,
Koto-ku, Tokyo 135-0061, Japan
www.renesas.com

Contact Information

For further information on a product, technology, the most up-to-date version of a document, or your nearest sales office, please visit:
www.renesas.com/contact/

Trademarks

Renesas and the Renesas logo are trademarks of Renesas Electronics Corporation. All trademarks and registered trademarks are the property of their respective owners.